

Fundamentals of power electronics for electric drives

Actuators - IRO6

Prof. Dr.-Ing. Mercedes Herranz Gracia

23.06.2024

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

And for electric drives?

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

And for electric drives?

- **DC servo motors** require variable DC voltage

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

And for electric drives?

- **DC servo motors** require variable DC voltage
 - DC converter for DC supply

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

And for electric drives?

- **DC servo motors** require variable DC voltage
 - DC converter for DC supply
 - Rectifier for AC supply

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

And for electric drives?

- **DC servo motors** require variable DC voltage
 - DC converter for DC supply
 - Rectifier for AC supply
- **Synchronous servo motors** require 3-phase variable AC voltage

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

And for electric drives?

- **DC servo motors** require variable DC voltage
 - DC converter for DC supply
 - Rectifier for AC supply
- **Synchronous servo motors** require 3-phase variable AC voltage
 - 3-phase inverter for DC supply

Task of power electronics

- Supply of electrotechnical devices (e.g. drives) with optimal voltage / frequency for optimum efficiency

4 different cases

- **Rectifiers**: AC voltage system at input, DC voltage system at output
- **Inverters**: DC voltage system at input, AC voltage system at output
- **Converters**: AC voltage system at the input and output (different input and output voltages/frequencies)
- **Regulators or DC converters**: DC voltage system at input and output (different input and output voltages)

And for electric drives?

- **DC servo motors** require variable DC voltage
 - DC converter for DC supply
 - Rectifier for AC supply
- **Synchronous servo motors** require 3-phase variable AC voltage
 - 3-phase inverter for DC supply
 - (3-phase) rectifier + 3-phase inverter for AC supply *3-phase 1-phase*

Use of power electronics

Power electronic devices control or regulate the flow of energy between producers and consumers:

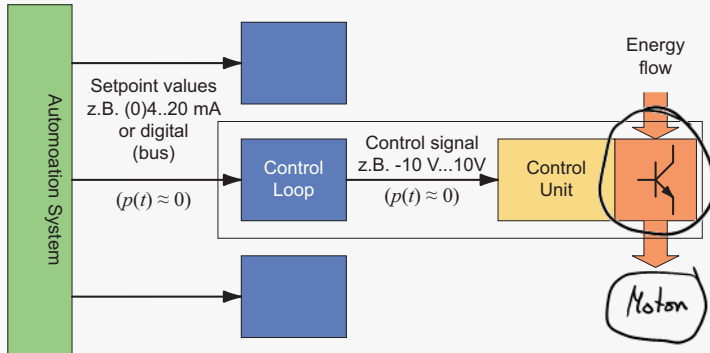


Figure Basic structure of power electronic devices



Fundamentals of power electronics for electric drives

- 1 Passive components as energy storage
- 2 Active components of power electronics
- 3 Idealization
- 4 Step-down converter (Buck-Converter)
- 5 Step-up converter (Boost-Converter)
- 6 Multi-quadrant controller
- 7 Modulation and Inverter

Capacitors , Inductors
as energy storage to
smooth the output
values (current and
voltage) of the circuit.

Passive components: coil as energy storage

Energy is stored in a (magnetic) coil:

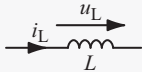
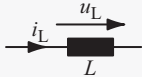


$$u_L(t) = L \frac{di_L}{dt}$$

Figure Voltage, current and energy of a coil

Passive components: coil as energy storage

Energy is stored in a (magnetic) coil:

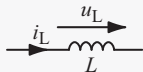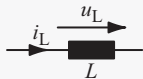



$$W_{\text{mag}} = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t u_L(\tau) i_L(\tau) d\tau = \int_{-\infty}^t L \frac{di_L}{d\tau} i_L(\tau) d\tau$$

$$u_L(t) = L \frac{di_L}{dt}$$

Figure Voltage, current and energy of a coil

Passive components: coil as energy storage

Energy is stored in a (magnetic) coil:

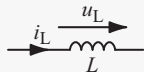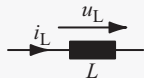


$$u_L(t) = L \frac{di_L}{dt}$$

$$\begin{aligned} W_{\text{mag}} &= \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t u_L(\tau) i_L(\tau) d\tau = \int_{-\infty}^t L \frac{di_L}{d\tau} i_L(\tau) d\tau \\ &= L \int_{i_L(-\infty)}^{i_L(t)} i_L(\tau) di_L = \frac{1}{2} L (i_L^2(t) - \underbrace{i_L^2(-\infty)}_{=0}) = \frac{1}{2} L i_L^2(t) \end{aligned}$$

Figure Voltage, current and energy of a coil

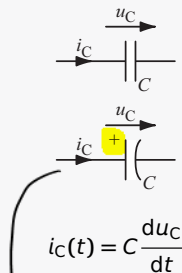Passive components: capacitor as energy storage



$$i_C(t) = C \frac{du_C}{dt}$$

$$\begin{aligned} W_{el} &= \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t i_C(\tau) u_C(\tau) d\tau = \int_{-\infty}^t C \frac{du_C}{d\tau} u_C(\tau) d\tau \\ &= C \int_{u_C(-\infty)}^{u_C(t)} u_C(\tau) du_C = \frac{1}{2} C (u_C^2(t) - \underbrace{u_C^2(-\infty)}_{=0}) = \frac{1}{2} C u_C^2(t) \end{aligned}$$

Figure Current, voltage and energy of a capacitor

Electrolytic capacitor.
 \Rightarrow Fixed direction of charge (always check before connecting)
 but with higher energy density (smaller for the same C)

Summary 1

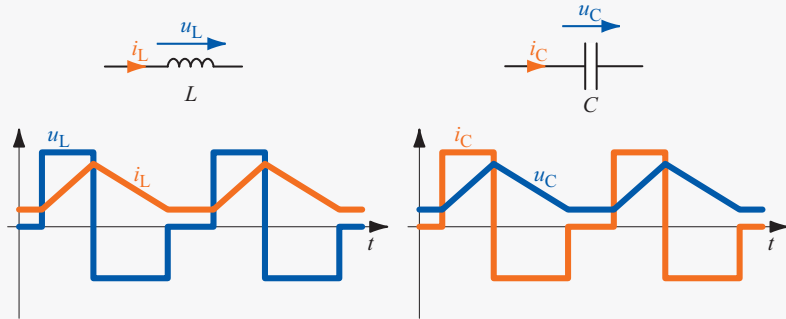


Figure Current and voltage curves with pulsed operation

Summary 2

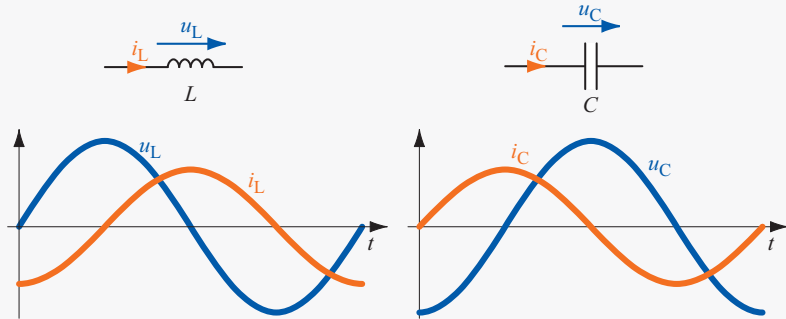


Figure Current and voltage curves with sinusoidal operation

Fundamentals of power electronics for electric drives

- 1 Passive components as energy storage
- 2 Active components of power electronics**
- 3 Idealization
- 4 Step-down converter (Buck-Converter)
- 5 Step-up converter (Boost-Converter)
- 6 Multi-quadrant controller
- 7 Modulation and Inverter

Active Components

- Non-controllable valves:
 - Diodes

Active Components

- Non-controllable valves:
 - Diodes
- Controllable valves:

Active Components

- Non-controllable valves:
 - Diodes
- Controllable valves:
 - Valves that can be switched on: thyristors

Active Components

- Non-controllable valves:
 - Diodes
- Controllable valves:
 - Valves that can be switched on: thyristors
 - Valves that can be switched on and off: transistors, IGBTs, MOSFETs

Active Components

- Non-controllable valves:
 - Diodes
- Controllable valves:
 - Valves that can be switched on: thyristors
 - Valves that can be switched on and off: transistors, IGBTs, MOSFETs

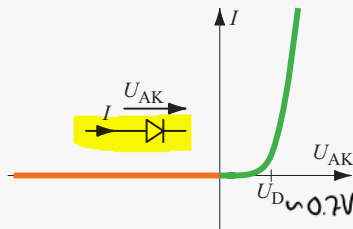


Figure Diode characteristic

Active Components

- Non-controllable valves:
 - Diodes
- Controllable valves:
 - Valves that can be switched on: thyristors
 - Valves that can be switched on and off: transistors, IGBTs, MOSFETs


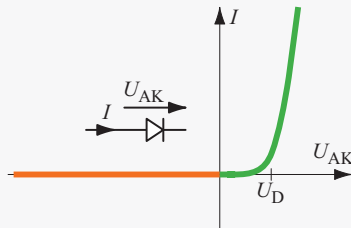


Figure Diode characteristic

Application: rectifier, fly-back diode

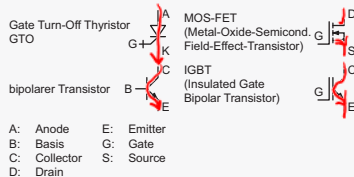
Active components: can be switched on and off



Similarities

- Conduct electricity in only one direction
- Can be switched on and off via auxiliary voltage
 - ON: $U_{GS} > 0$ (MOSFETs) / $U_{GE} > 0$ (IGBTs)
 - OFF: $U_{GS} \approx 0$ (MOSFETs) / $U_{GE} \approx 0$ (IGBTs)
- State-of-the-art Si components
- SiC and GaN in industrialization

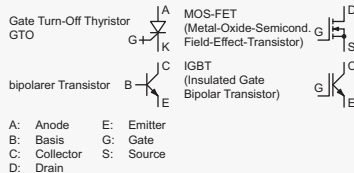Active components: can be switched on and off




■ GTO

- similar to normal thyristor
- can be switched off
- switching frequencies 200...400 Hz
- only in legacy systems

Similarities

- Conduct electricity in only one direction
- Can be switched on and off via auxiliary voltage
 - ON: $U_{GS} > 0$ (MOSFETs) / $U_{GE} > 0$ (IGBTs)
 - OFF: $U_{GS} \approx 0$ (MOSFETs) / $U_{GE} \approx 0$ (IGBTs)
- State-of-the-art Si components
- SiC and GaN in industrialization

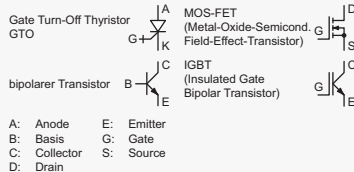Active components: can be switched on and off



Similarities

- Conduct electricity in only one direction
- Can be switched on and off via auxiliary voltage
 - ON: $U_{GS} > 0$ (MOSFETs) / $U_{GE} > 0$ (IGBTs)
 - OFF: $U_{GS} \approx 0$ (MOSFETs) / $U_{GE} \approx 0$ (IGBTs)
- State-of-the-art Si components
- SiC and GaN in industrialization


■ GTO

- similar to normal thyristor
- can be switched off
- switching frequencies 200...400 Hz
- only in legacy systems

■ Bip. transistor

- due to high switching losses only for very low power

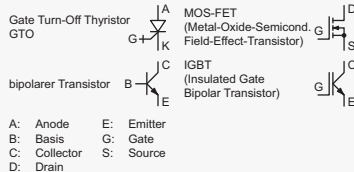Active components: can be switched on and off




Similarities

- Conduct electricity in only one direction
- Can be switched on and off via auxiliary voltage
 - ON: $U_{GS} > 0$ (MOSFETs) / $U_{GE} > 0$ (IGBTs)
 - OFF: $U_{GS} \approx 0$ (MOSFETs) / $U_{GE} \approx 0$ (IGBTs)
- State-of-the-art Si components
- SiC and GaN in industrialization

- GTO
 - similar to normal thyristor
 - can be switched off
 - switching frequencies 200...400 Hz
 - only in legacy systems
- Bip. transistor
 - due to high switching losses only for very low power
- MOSFET
 - small forward resistance
 - medium power range
 - power supplies for electronic devices, ...

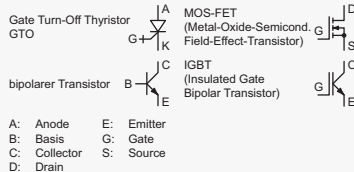Active components: can be switched on and off



Similarities

- Conduct electricity in only one direction
- Can be switched on and off via auxiliary voltage
 - ON: $U_{GS} > 0$ (MOSFETs) / $U_{GE} > 0$ (IGBTs)
 - OFF: $U_{GS} \approx 0$ (MOSFETs) / $U_{GE} \approx 0$ (IGBTs)
- State-of-the-art Si components
- SiC and GaN in industrialization

GTO

- similar to normal thyristor
- can be switched off
- switching frequencies 200...400 Hz
- only in legacy systems

Bip. transistor

- due to high switching losses only for very low power

MOSFET

- small forward resistance
- medium power range
- power supplies for electronic devices, ...

IGBT

- greater dielectric strength
- high voltage systems
- outputs up to 2 MW

← For motor drives for voltages $\leq 100V$

← For motor drives for voltages $> 100V$

Fundamentals of power electronics for electric drives

- 1 Passive components as energy storage
- 2 Active components of power electronics
- 3 Idealization**
- 4 Step-down converter (Buck-Converter)
- 5 Step-up converter (Boost-Converter)
- 6 Multi-quadrant controller
- 7 Modulation and Inverter

Idealized Theory

- Considered semiconductor elements:
 - only valves that can be switched on and off (IGBT/MOSFET) and diodes

Idealized Theory

- Considered semiconductor elements:
 - only valves that can be switched on and off (IGBT/MOSFET) and diodes
 - ideal switches
($u_V(t) = 0$ in the conducting state, $i_V(t) = 0$ in blocking state),
 - Switching times are negligible (i.e. sudden commutation)

Idealized Theory

- Considered semiconductor elements:
 - only valves that can be switched on and off (IGBT/MOSFET) and diodes
 - ideal switches
($u_V(t) = 0$ in the conducting state, $i_V(t) = 0$ in blocking state),
 - Switching times are negligible (i.e. sudden commutation)
- Internal resistances and impedances are neglected

Idealized Theory

- Considered semiconductor elements:
 - only valves that can be switched on and off (IGBT/MOSFET) and diodes
 - ideal switches
($u_V(t) = 0$ in the conducting state, $i_V(t) = 0$ in blocking state),
 - Switching times are negligible (i.e. sudden commutation)
- Internal resistances and impedances are neglected
- Input voltage U_1 and output voltage U_2 are constant

Idealized Theory

- Considered semiconductor elements:
 - only valves that can be switched on and off (IGBT/MOSFET) and diodes
 - ideal switches
($u_V(t) = 0$ in the conducting state, $i_V(t) = 0$ in blocking state),
 - Switching times are negligible (i.e. sudden commutation)
- Internal resistances and impedances are neglected
- Input voltage U_1 and output voltage U_2 are constant
- Only steady state
 - ⇒ periodic time functions for current and voltage
 - ⇒ $\overline{u_L(t)} = 0$ and $\overline{i_C(t)} = 0$!

$$u_L = L \cdot \frac{di_L}{dt} \quad i_C = C \cdot \frac{du_C}{dt}$$

Idealized Theory

- Considered semiconductor elements:
 - only valves that can be switched on and off (IGBT/MOSFET) and diodes
 - ideal switches
($u_V(t) = 0$ in the conducting state, $i_V(t) = 0$ in blocking state),
 - Switching times are negligible (i.e. sudden commutation)
- Internal resistances and impedances are neglected
- Input voltage U_1 and output voltage U_2 are constant
- Only steady state
 - ⇒ periodic time functions for current and voltage
 - ⇒ $\overline{u_L(t)} = 0$ and $\overline{i_C(t)} = 0$!
- Inductivities: initially infinitely large, i.e. practical $L \rightarrow \infty$
 - ⇒ Current through the inductance $i_L = \text{const.}$, i.e. without alternating component

Idealized Theory

- Usual procedure for sizing of power electronic devices:
 - idealized study
 - ideal switches, $L, C \rightarrow \infty$

Idealized Theory

- Usual procedure for sizing of power electronic devices:
 - idealized study
→ ideal switches, $L, C \rightarrow \infty$
 - simplified study
→ switches with forward voltage and resistance, $L, C < \infty$

Idealized Theory

- Usual procedure for sizing of power electronic devices:
 - idealized study
 - ideal switches, $L, C \rightarrow \infty$
 - simplified study
 - switches with forward voltage and resistance, $L, C < \infty$
 - detailed study
 - switch with real characteristic, $L, C < \infty, L = f(I)$

Idealized Theory

- Usual procedure for sizing of power electronic devices:
 - idealized study
→ ideal switches, $L, C \rightarrow \infty$
 - simplified study
→ switches with forward voltage and resistance, $L, C < \infty$
 - detailed study
→ switch with real characteristic, $L, C < \infty, L = f(I)$

Next content:

- buck converter

Idealized Theory

- Usual procedure for sizing of power electronic devices:
 - idealized study
→ ideal switches, $L, C \rightarrow \infty$
 - simplified study
→ switches with forward voltage and resistance, $L, C < \infty$
 - detailed study
→ switch with real characteristic, $L, C < \infty, L = f(I)$


Next content:

- buck converter
- boost converter
- inverse converter (buck/boost converter)

Idealized Theory

- Usual procedure for sizing of power electronic devices:
 - idealized study
→ ideal switches, $L, C \rightarrow \infty$
 - simplified study
→ switches with forward voltage and resistance, $L, C < \infty$
 - detailed study
→ switch with real characteristic, $L, C < \infty, L = f(I)$

Next content:


- 
- buck converter
 - boost converter
 - inverse converter (buck/boost converter)
 - half bridge
 - four-quadrant controller (full bridge) \Rightarrow DC servo controller
 - (three-phase) inverter (inverter) \Rightarrow AC servo controller

Fundamentals of power electronics for electric drives

- 1 Passive components as energy storage
- 2 Active components of power electronics
- 3 Idealization
- 4 Step-down converter (Buck-Converter)**
- 5 Step-up converter (Boost-Converter)
- 6 Multi-quadrant controller
- 7 Modulation and Inverter


Step-down converter

- Switch S on and off periodically

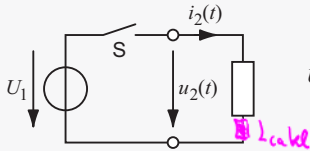

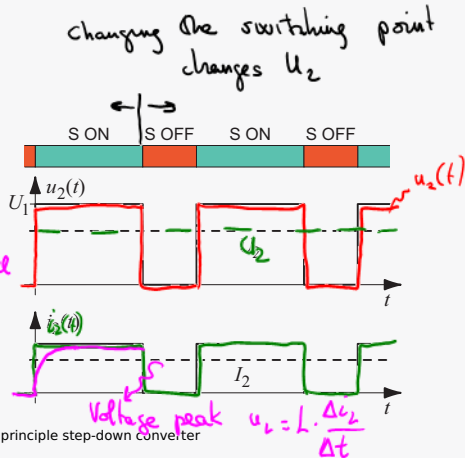Problems with this circuit

- ① $u_2(t)$ pulsates
- ② $i_2(t)$ pulsates
- ③ Parasitic inductance of cables



Step-down converter

- Switch S on and off periodically
- DC voltage U_1 → pulsed output voltage $u_2(t)$

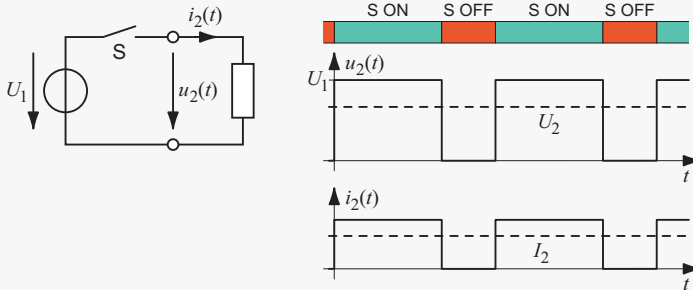


Figure Basic principle step-down converter

Step-down converter

- Switch S on and off periodically
- DC voltage $U_1 \rightarrow$ pulsed output voltage $u_2(t)$
- Average output voltage $U_2 = \overline{u_2(t)} < \text{Input voltage } U_1$

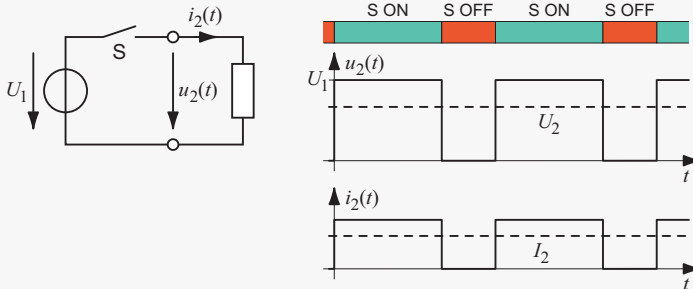


Figure Basic principle step-down converter

Step-down converter

- Switch S on and off periodically
- DC voltage $U_1 \rightarrow$ pulsed output voltage $u_2(t)$
- Average output voltage $U_2 = \overline{u_2(t)} < \text{Input voltage } U_1$
- with a purely resistive load $i_2(t) \sim u_2(t)$

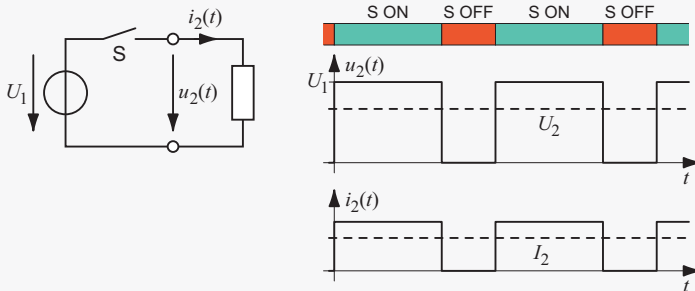


Figure Basic principle step-down converter

Trouble switching off

Mechanical switch: switching spark when switching off depends on

- size of the current to be switched off
- speed of switching off

Trouble switching off

Mechanical switch: switching spark when switching off depends on

- size of the current to be switched off
- speed of switching off

Current-carrying conductor:

- always has a magnetic field:
E.g. wire: inductance of approx. 10 nH/cm

Trouble switching off

Mechanical switch: switching spark when switching off depends on

- size of the current to be switched off
- speed of switching off

Current-carrying conductor:

- always has a magnetic field:
E.g. wire: inductance of approx. 10 nH/cm

Example: Power from 100 A is cut off within 100 ns

$$u_{\text{wire}} = L \cdot \frac{di_{\text{wire}}}{dt} = 100 \text{ nH/cm} \cdot \frac{100 \text{ A}}{100 \text{ ns}} = 100 \text{ V/cm}$$

⇒ Flyback diode to avoid this problem

Fly-back Diode

- Loading with an inductive part
 - ⇒ Load current cannot be abruptly reduced
 - ⇒ **Fly-back diode** in parallel with the load for protection:

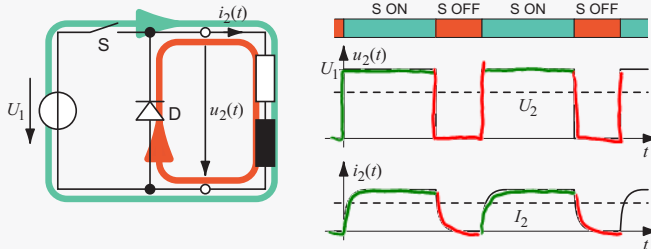


Figure Basic principle step-down converter with fly-back diode

Fly-back Diode

- Loading with an inductive part
 - ⇒ Load current cannot be abruptly reduced
 - ⇒ **Fly-back diode** in parallel with the load for protection:

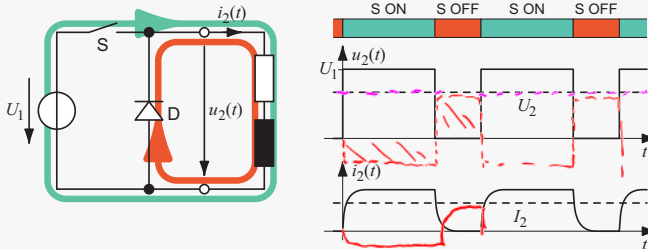


Figure Basic principle step-down converter with fly-back diode

- Switch opens:
 - ⇒ Circuit remains closed via load and fly-back diode

Problems

- ① Pulsating voltage $u_2(t)$
- ② Non-constant output current $i_2(t)$

Fly-back Diode

- Loading with an inductive part
 - ⇒ Load current cannot be abruptly reduced
 - ⇒ **Fly-back diode** in parallel with the load for protection:

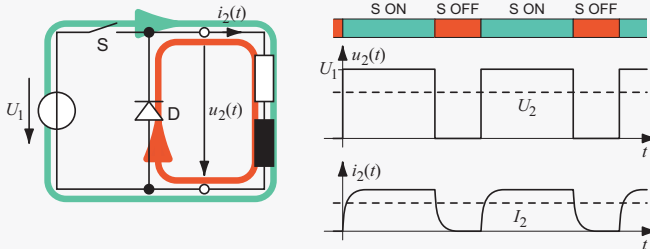


Figure Basic principle step-down converter with fly-back diode

- Switch opens:
 - ⇒ Circuit remains closed via load and fly-back diode
 - ⇒ Energy stored in inductor → Heat loss in the resistor

Smoothing inductance and output capacitor

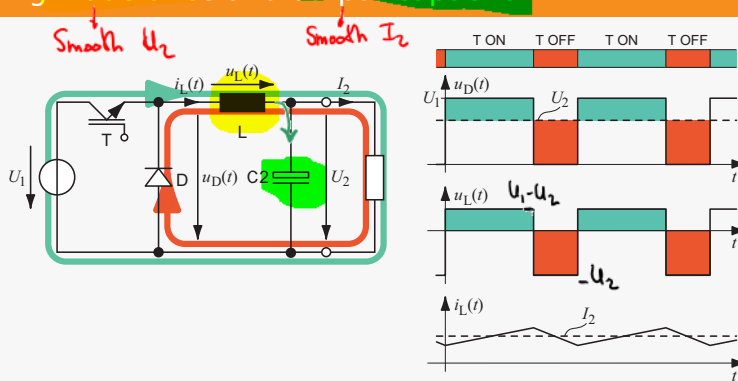


Figure Step-down converter with fly-back diode, smoothing inductance and output capacitor

$$u_o(t) = U_2 + u_L(t) \rightarrow u_L(t) = u_o(t) - U_2$$

$\begin{cases} T \text{ ON} \rightarrow u_o(t) = U_1 \rightarrow u_L(t) = U_1 - U_2 \\ T \text{ OFF} \rightarrow u_o(t) = 0 \rightarrow u_L(t) = -U_2 \end{cases}$

Smoothing inductance and output capacitor

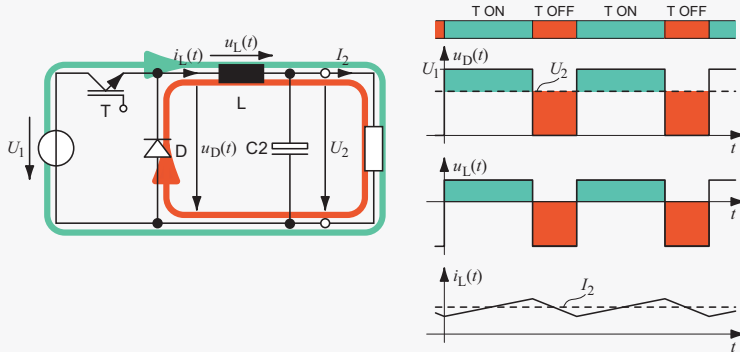


Figure Step-down converter with fly-back diode, smoothing inductance and output capacitor

- L takes up the alternating part of $u_D(t)$: $\overline{u_D(t)} - U_2 = u_L(t)$

Smoothing inductance and output capacitor

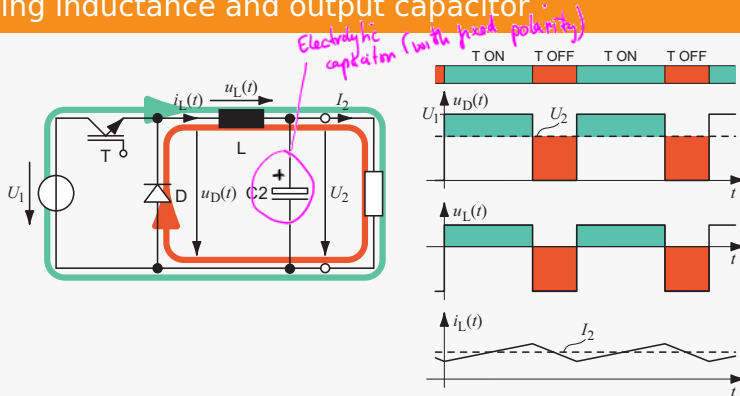


Figure Step-down converter with fly-back diode, smoothing inductance and output capacitor

- L takes up the alternating part of $u_D(t)$: $\overline{u_D(t)} - U_2 = u_L(t)$
- C_2 takes up the alternating part of $i_L(t)$: $\overline{i_L(t)} - I_2 = i_{C2}(t)$

Input Capacitor?

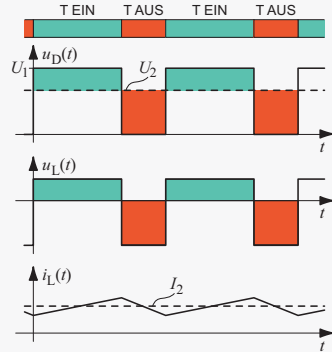
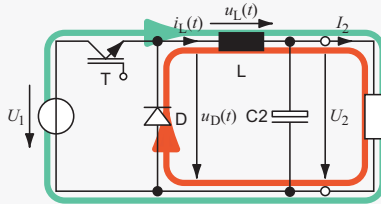


Figure Step-down converter with fly-back diode, smoothing inductance and output capacitor

Input Capacitor?

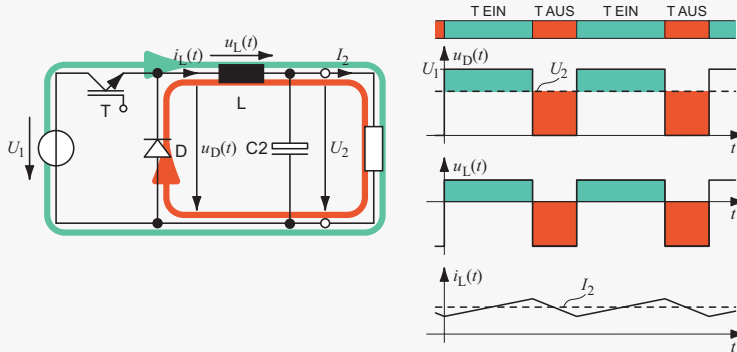


Figure Step-down converter with fly-back diode, smoothing inductance and output capacitor

- Collector current (= input current I_1) jumps!

Input Capacitor?


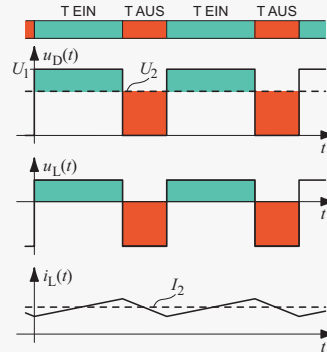
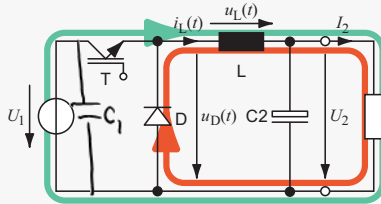



Figure Step-down converter with fly-back diode, smoothing inductance and output capacitor

- Collector current (= input current I_1) jumps!
- ⇒ Input capacitor to protect T necessary!


Step-down converter

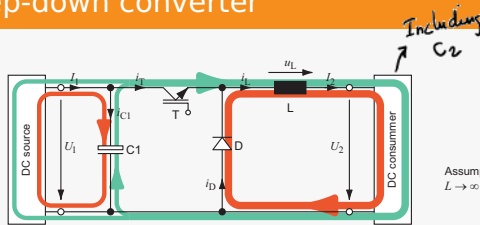

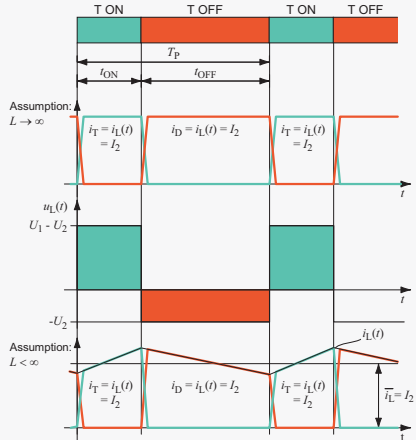■ $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$




Step-down converter

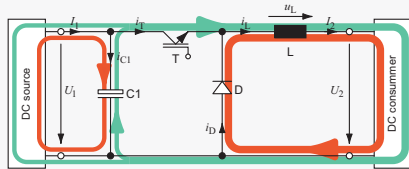


■ $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$

■ $U_2 \leq U_1$ or $I_2 \geq I_1$

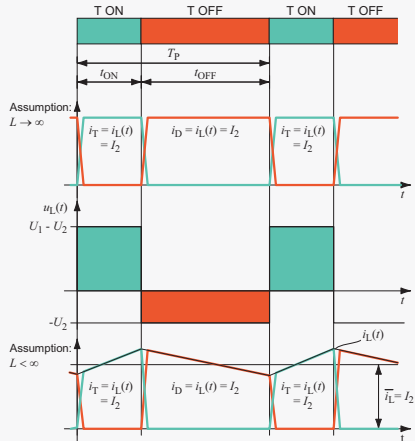Power balance: $U_1 \cdot I_1 = U_2 \cdot I_2$
 $\Rightarrow I_2 \geq I_1$



Step-down converter

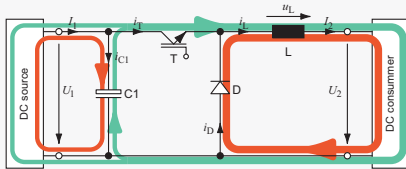


■ $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$


■ $U_2 \leq U_1$ or $I_2 \geq I_1$

■ ON state:


■ OFF state:

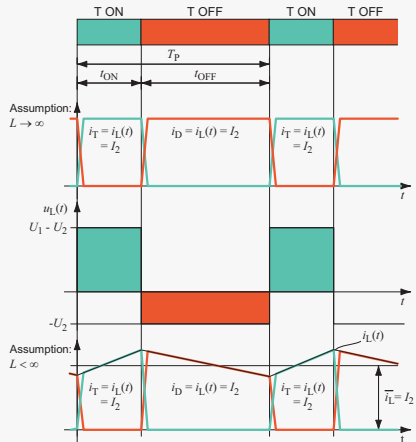


Step-down converter

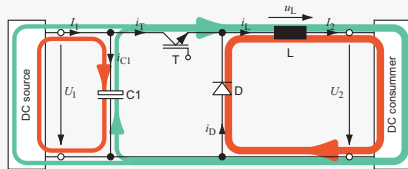

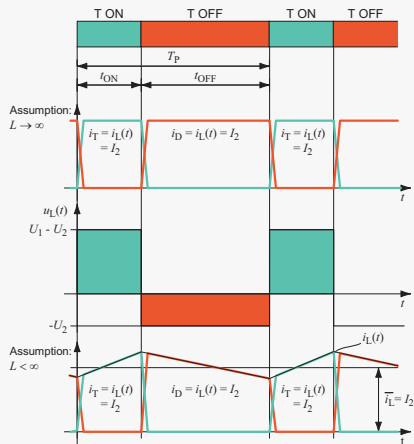
- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \leq U_1$ or $I_2 \geq I_1$
- ON state: I_2
 - $I_1 - i_T = i_{C1} \rightarrow i_{C1} = I_1 - I_2 < 0$
- OFF state:




Step-down converter

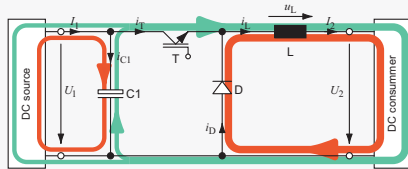

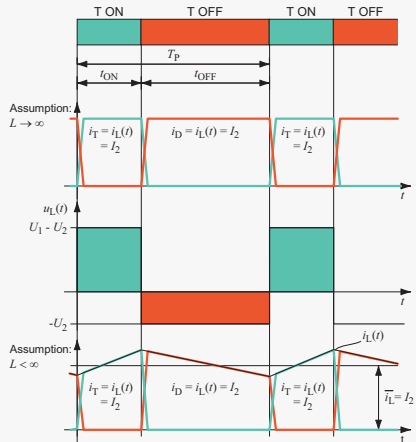
- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \leq U_1$ or $I_2 \geq I_1$
- ON state:
 - $I_1 - i_T = i_{C1} \rightarrow i_{C1} = I_1 - I_2 < 0$
- OFF state:
 - $I_1 - i_D = i_{C1} \rightarrow i_{C1} = I_1 > 0$




Step-down converter

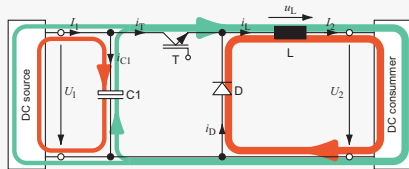

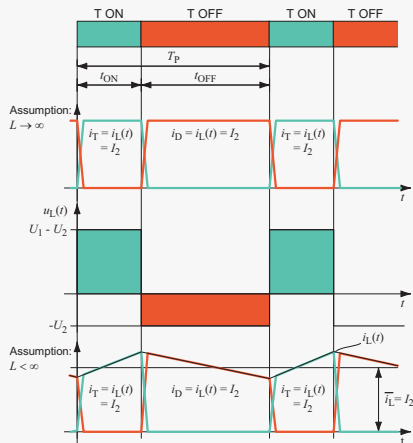
- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \leq U_1$ or $I_2 \geq I_1$
- ON state:
 - $I_1 - i_T = i_{C1} \rightarrow i_{C1} = I_1 - I_2 < 0$
- OFF state:
 - $I_1 - i_T = i_{C1} \rightarrow i_{C1} = I_1 > 0$
 - ⇒ C_1 takes the charge $I_1 \cdot t_{\text{OFF}}$



Step-down converter

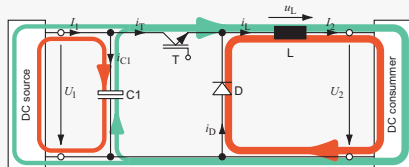

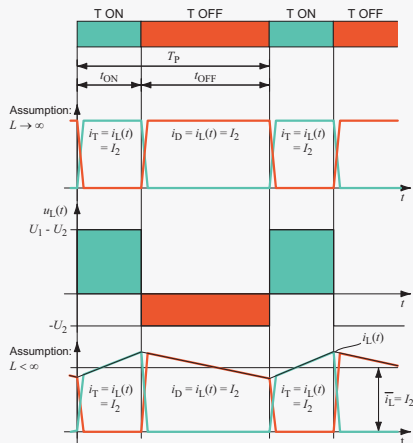- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \leq U_1$ or $I_2 \geq I_1$
- ON state:
 - $I_1 - i_T = i_{C1} \rightarrow i_{C1} = I_1 - I_2 < 0$
 - ⇒ C_1 gives the charge $(I_2 - I_1) \cdot t_{\text{ON}}$
- OFF state:
 - $I_1 - i_T = i_{C1} \rightarrow i_{C1} = I_1 > 0$
 - ⇒ C_1 takes the charge $I_1 \cdot t_{\text{OFF}}$



Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}}$$

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_2 \cdot t_{\text{ON}} = I_1 \cdot \overbrace{(t_{\text{OFF}} + t_{\text{ON}})}^{T_p}$$

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \Rightarrow I_2 \cdot t_{\text{ON}} = I_1 \cdot (t_{\text{OFF}} + t_{\text{ON}}) \Rightarrow I_1 = I_2 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot I_2$$

Duty cycle
↓
Relative ON-Time in
a period

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \Rightarrow I_2 \cdot t_{\text{ON}} = I_1 \cdot (t_{\text{OFF}} + t_{\text{ON}}) \Rightarrow I_1 = I_2 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot I_2$$

ON state ($u_D(t) = U_1$):

$$-U_1 + u_L(t) + U_2 = 0 \Rightarrow u_L(t) = U_1 - U_2$$

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \Rightarrow I_2 \cdot t_{\text{ON}} = I_1 \cdot (t_{\text{OFF}} + t_{\text{ON}}) \Rightarrow I_1 = I_2 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot I_2$$

ON state ($u_D(t) = U_1$):

$$-U_1 + u_L(t) + U_2 = 0 \Rightarrow u_L(t) = U_1 - U_2$$

OFF state ($u_D(t) = 0$):

$$u_L(t) + U_2 = 0 \Rightarrow u_L(t) = -U_2$$

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \Rightarrow I_2 \cdot t_{\text{ON}} = I_1 \cdot (t_{\text{OFF}} + t_{\text{ON}}) \Rightarrow I_1 = I_2 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot I_2$$

ON state ($u_D(t) = U_1$):

$$-U_1 + u_L(t) + U_2 = 0 \Rightarrow u_L(t) = U_1 - U_2$$

OFF state ($u_D(t) = 0$):

$$u_L(t) + U_2 = 0 \Rightarrow u_L(t) = -U_2$$

$$\overline{u_L(t)} = 0 \Rightarrow (U_1 - U_2) \cdot t_{\text{ON}} - U_2 \cdot t_{\text{OFF}} = 0$$

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \Rightarrow I_2 \cdot t_{\text{ON}} = I_1 \cdot (t_{\text{OFF}} + t_{\text{ON}}) \Rightarrow I_1 = I_2 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot I_2$$

ON state ($u_D(t) = U_1$):

$$-U_1 + u_L(t) + U_2 = 0 \Rightarrow u_L(t) = U_1 - U_2$$

OFF state ($u_D(t) = 0$):

$$u_L(t) + U_2 = 0 \Rightarrow u_L(t) = -U_2$$

$$\overline{u_L(t)} = 0 \Rightarrow (U_1 - U_2) \cdot t_{\text{ON}} - U_2 \cdot t_{\text{OFF}} = 0 \Rightarrow U_1 \cdot t_{\text{ON}} = U_2 \cdot T_P \Rightarrow U_2 = U_1 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot U_1$$

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \Rightarrow I_2 \cdot t_{\text{ON}} = I_1 \cdot (t_{\text{OFF}} + t_{\text{ON}}) \Rightarrow I_1 = I_2 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot I_2$$

ON state ($u_D(t) = U_1$):

$$-U_1 + u_L(t) + U_2 = 0 \Rightarrow u_L(t) = U_1 - U_2$$

OFF state ($u_D(t) = 0$):

$$u_L(t) + U_2 = 0 \Rightarrow u_L(t) = -U_2$$

$$\overline{u_L(t)} = 0 \Rightarrow (U_1 - U_2) \cdot t_{\text{ON}} - U_2 \cdot t_{\text{OFF}} = 0 \Rightarrow U_1 \cdot t_{\text{ON}} = U_2 \cdot T_P \Rightarrow U_2 = U_1 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot U_1$$

$$U_1 \cdot I_1 = U_1 \cdot \overline{i_T(t)} = U_2 \cdot I_2$$

Step-down converter

$$(I_2 - I_1) \cdot t_{\text{ON}} = I_1 \cdot t_{\text{OFF}} \Rightarrow I_2 \cdot t_{\text{ON}} = I_1 \cdot (t_{\text{OFF}} + t_{\text{ON}}) \Rightarrow I_1 = I_2 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot I_2$$

ON state ($u_D(t) = U_1$):

$$-U_1 + u_L(t) + U_2 = 0 \Rightarrow u_L(t) = U_1 - U_2$$

OFF state ($u_D(t) = 0$):

$$u_L(t) + U_2 = 0 \Rightarrow u_L(t) = -U_2$$



$$\overline{u_L(t)} = 0 \Rightarrow (U_1 - U_2) \cdot t_{\text{ON}} - U_2 \cdot t_{\text{OFF}} = 0 \Rightarrow U_1 \cdot t_{\text{ON}} = U_2 \cdot T_P \Rightarrow U_2 = U_1 \cdot \frac{t_{\text{ON}}}{T_P} = D \cdot U_1$$

$$U_1 \cdot I_1 = U_1 \cdot \overline{i_T(t)} = U_2 \cdot I_2$$


next step with $L < \infty$:

$$u_L(t) = L \cdot \frac{di_L}{dt}$$


Step-down converter with $L < \infty$

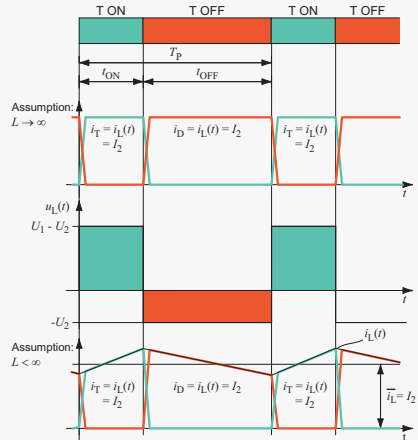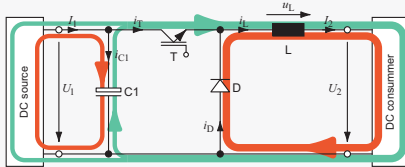


Step-down converter with $L < \infty$

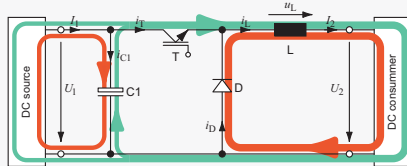

■ ON state:

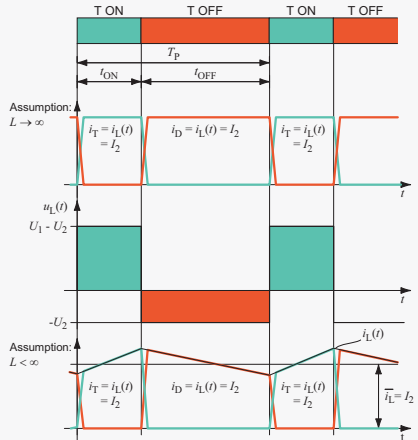


Step-down converter with $L < \infty$

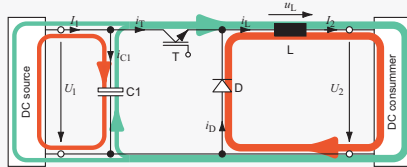


■ ON state:
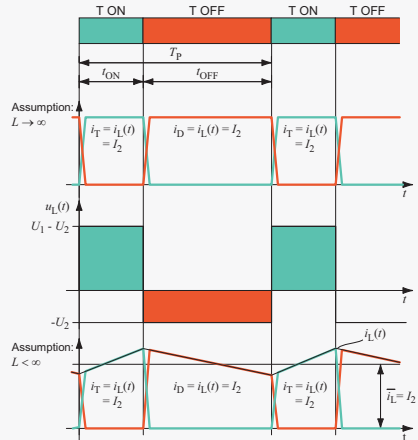
$$\blacksquare u_L(t) = U_1 - U_2 = L \cdot \frac{di_L}{dt}$$




Step-down converter with $L < \infty$

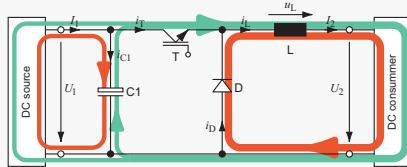


■ ON state:

$$\blacksquare u_L(t) = U_1 - U_2 = L \cdot \frac{di_L}{dt}$$

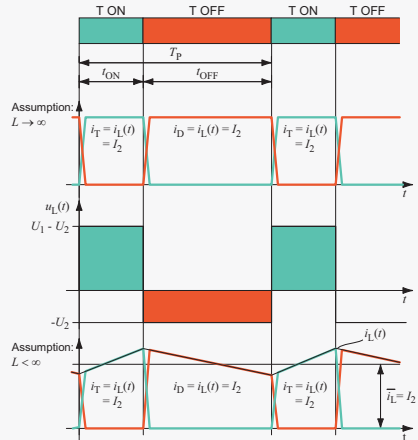
$$\Rightarrow \frac{di_L}{dt} > 0 \text{ and constant}$$




Step-down converter with $L < \infty$

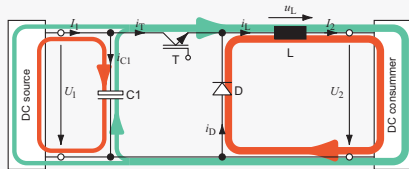

- OFF state:

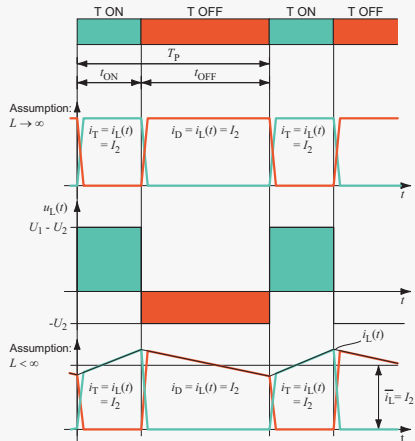

Step-down converter with $L < \infty$

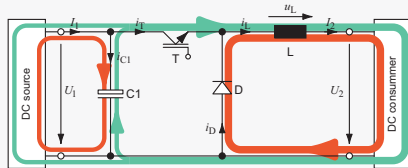


ON state:

$$u_L(t) = U_1 - U_2 = L \cdot \frac{di_L}{dt}$$


$$\Rightarrow \frac{di_L}{dt} > 0 \text{ and constant}$$

OFF state:
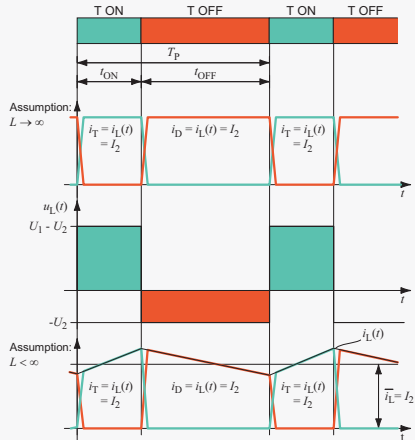
$$u_L(t) = -U_2 = L \cdot \frac{di_L}{dt}$$



Step-down converter with $L < \infty$

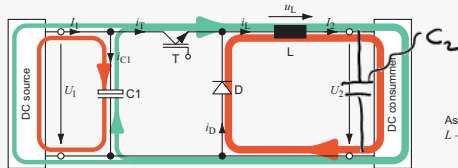

ON state:


$$u_L(t) = U_1 - U_2 = L \cdot \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} > 0 \text{ and constant}$$

OFF state:

$$u_L(t) = -U_2 = L \cdot \frac{di_L}{dt}$$

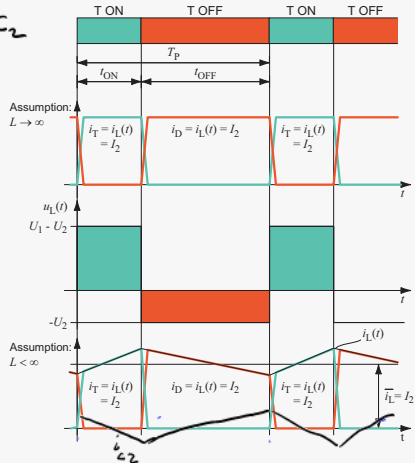
$$\Rightarrow \frac{di_L}{dt} < 0 \text{ and constant}$$




Fundamentals of power electronics for electric drives

- 1 Passive components as energy storage
- 2 Active components of power electronics
- 3 Idealization
- 4 Step-down converter (Buck-Converter)
- 5 Step-up converter (Boost-Converter)**
- 6 Multi-quadrant controller
- 7 Modulation and Inverter


Step-up converter

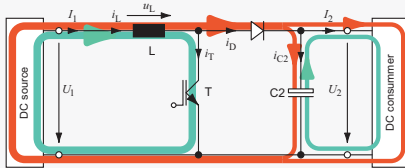

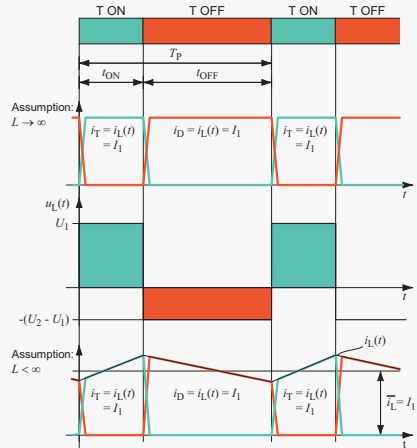■ $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$




Step-up converter

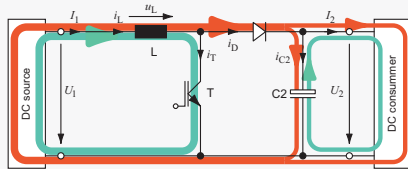


■ $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$

■ $U_2 \geq U_1$ or $I_2 \leq I_1$

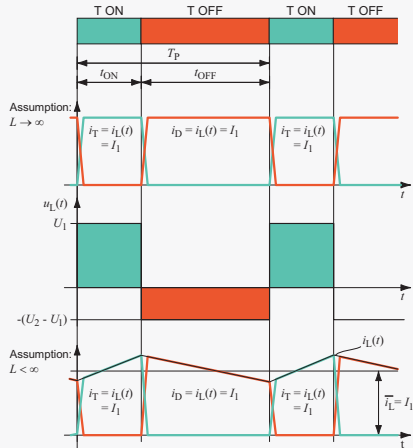
On the ON-State, L is charged.
 On the OFF state L must
 discharge \Rightarrow Increasing
 the output voltage.




Step-up converter

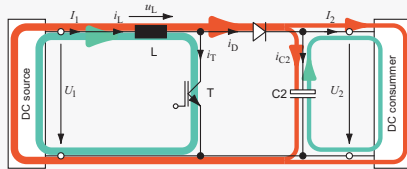

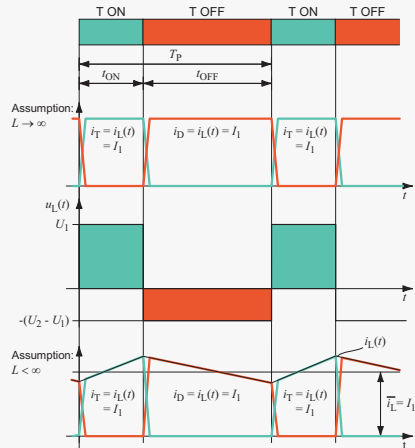
- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \geq U_1$ or $I_2 \leq I_1$
- ON state:
- OFF state:




Step-up converter

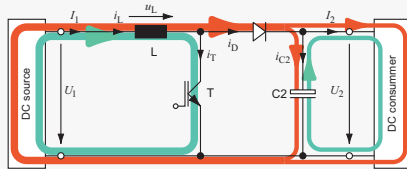

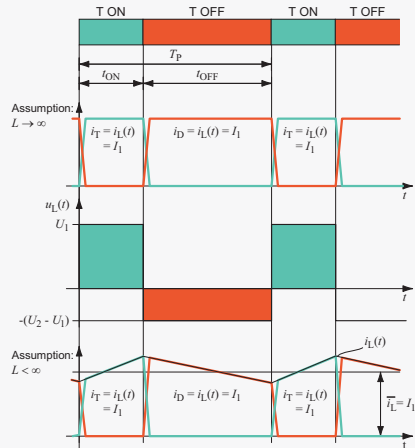
- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \geq U_1$ or $I_2 \leq I_1$
- ON state:
 - $0 = I_2 + i_{C2} \rightarrow i_{C2} = -I_2 < 0$
- OFF state:




Step-up converter

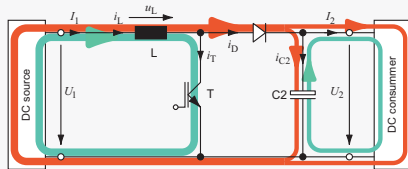

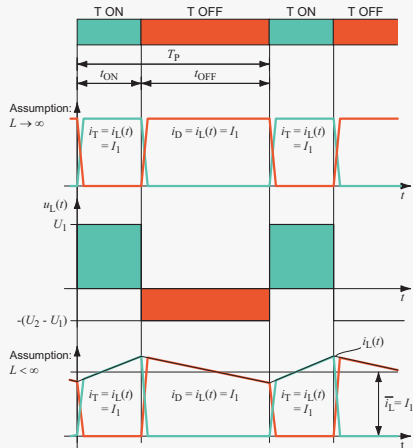
- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \geq U_1$ or $I_2 \leq I_1$
- ON state:
 - $0 = I_2 + i_{C2} \rightarrow i_{C2} = -I_2 < 0$
- OFF state:
 - $I_1 = I_2 + i_{C2} \rightarrow i_{C2} = I_1 - I_2 > 0$




Step-up converter

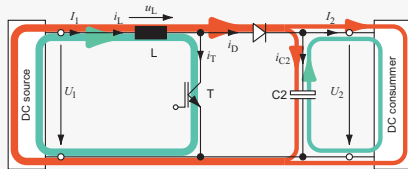

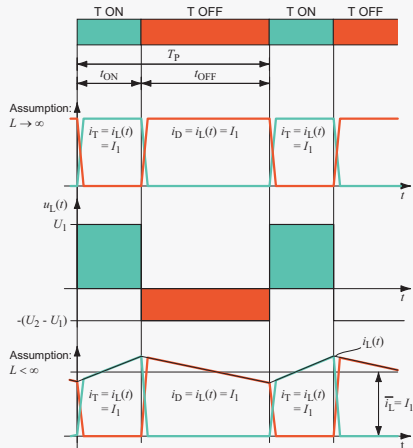
- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \geq U_1$ or $I_2 \leq I_1$
- ON state:
 - $0 = I_2 + i_{C2} \rightarrow i_{C2} = -I_2 < 0$
- OFF state:
 - $I_1 = I_2 + i_{C2} \rightarrow i_{C2} = I_1 - I_2 > 0$
 - ➔ C_2 takes up the charge $(I_1 - I_2) \cdot t_{\text{OFF}}$



Step-up converter

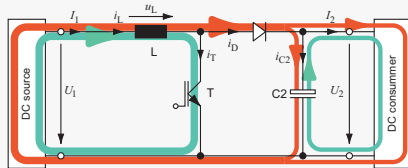

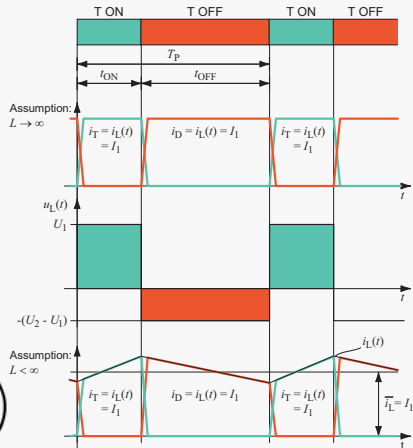- $L \rightarrow \infty: i_L(t) = I_2 = \text{const.}$
- $U_2 \geq U_1$ or $I_2 \leq I_1$
- ON state:
 - $0 = I_2 + i_{C2} \rightarrow i_{C2} = -I_2 < 0$
 - ➔ C_2 gives off the charge $I_2 \cdot t_{\text{ON}}$
- OFF state:
 - $I_1 = I_2 + i_{C2} \rightarrow i_{C2} = I_1 - I_2 > 0$
 - ➔ C_2 takes up the charge $(I_1 - I_2) \cdot t_{\text{OFF}}$



Step-up converter

$$I_2 \cdot t_{\text{ON}} = (I_1 - I_2) \cdot t_{\text{OFF}}$$

Step-up converter

$$I_2 \cdot t_{\text{ON}} = (I_1 - I_2) \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_1 \cdot t_{\text{OFF}} = I_2 \cdot (t_{\text{ON}} + t_{\text{OFF}})$$

Step-up converter

$$\begin{aligned} I_2 \cdot t_{\text{ON}} &= (I_1 - I_2) \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_1 \cdot t_{\text{OFF}} = I_2 \cdot (t_{\text{ON}} + t_{\text{OFF}}) \\ \Rightarrow \quad I_2 &= I_1 \cdot \frac{\overbrace{T_P - t_{\text{ON}}}^{t_{\text{OFF}}}}{T_P} = (1 - D) \cdot I_1 \end{aligned}$$

Step-up converter

$$I_2 \cdot t_{\text{ON}} = (I_1 - I_2) \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_1 \cdot t_{\text{OFF}} = I_2 \cdot (t_{\text{ON}} + t_{\text{OFF}})$$

$$\Rightarrow \quad I_2 = I_1 \cdot \frac{T_P - t_{\text{ON}}}{T_P} = (1 - D) \cdot I_1$$

ON state ($u_{\text{CE}}(t) = U_1$):

$$-U_1 + u_{\text{L}}(t) = 0 \quad \Rightarrow \quad u_{\text{L}}(t) = U_1$$

Step-up converter

$$I_2 \cdot t_{\text{ON}} = (I_1 - I_2) \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_1 \cdot t_{\text{OFF}} = I_2 \cdot (t_{\text{ON}} + t_{\text{OFF}})$$

$$\Rightarrow \quad I_2 = I_1 \cdot \frac{T_P - t_{\text{ON}}}{T_P} = (1 - D) \cdot I_1$$

ON state ($u_{\text{CE}}(t) = U_1$):

$$-U_1 + u_{\text{L}}(t) = 0 \quad \Rightarrow \quad u_{\text{L}}(t) = U_1$$

OFF state ($u_{\text{CE}}(t) = U_2$):

$$-U_1 + u_{\text{L}}(t) + U_2 = 0 \quad \Rightarrow \quad u_{\text{L}}(t) = -(U_2 - U_1)$$

Step-up converter

$$I_2 \cdot t_{\text{ON}} = (I_1 - I_2) \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_1 \cdot t_{\text{OFF}} = I_2 \cdot (t_{\text{ON}} + t_{\text{OFF}})$$

$$\Rightarrow \quad I_2 = I_1 \cdot \frac{T_P - t_{\text{ON}}}{T_P} = (1 - D) \cdot I_1$$

ON state ($u_{\text{CE}}(t) = U_1$):

$$-U_1 + u_{\text{L}}(t) = 0 \quad \Rightarrow \quad u_{\text{L}}(t) = U_1$$

OFF state ($u_{\text{CE}}(t) = U_2$):

$$-U_1 + u_{\text{L}}(t) + U_2 = 0 \quad \Rightarrow \quad u_{\text{L}}(t) = -(U_2 - U_1)$$

$$\overline{u_{\text{L}}(t)} = 0 = \frac{U_1 \cdot t_{\text{ON}} - (U_2 - U_1) \cdot t_{\text{OFF}}}{T_P} \quad \Rightarrow \quad (U_2 - U_1) \cdot t_{\text{OFF}} = U_1 \cdot t_{\text{ON}}$$

Step-up converter

$$I_2 \cdot t_{\text{ON}} = (I_1 - I_2) \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_1 \cdot t_{\text{OFF}} = I_2 \cdot (t_{\text{ON}} + t_{\text{OFF}})$$

$$\Rightarrow \quad I_2 = I_1 \cdot \frac{T_P - t_{\text{ON}}}{T_P} = (1 - D) \cdot I_1$$

ON state ($u_{\text{CE}}(t) = U_1$):

$$-U_1 + u_{\text{L}}(t) = 0 \quad \Rightarrow \quad u_{\text{L}}(t) = U_1$$

OFF state ($u_{\text{CE}}(t) = U_2$):

$$-U_1 + u_{\text{L}}(t) + U_2 = 0 \quad \Rightarrow \quad u_{\text{L}}(t) = -(U_2 - U_1)$$

$$\overline{u_{\text{L}}(t)} = 0 = \frac{U_1 \cdot t_{\text{ON}} - (U_2 - U_1) \cdot t_{\text{OFF}}}{T_P} \quad \Rightarrow \quad (U_2 - U_1) \cdot t_{\text{OFF}} = U_1 \cdot t_{\text{ON}}$$

$$\Rightarrow \quad U_2 = U_1 \cdot \frac{t_{\text{OFF}} + t_{\text{ON}}}{t_{\text{OFF}}} = \frac{T_P}{t_{\text{OFF}}} \cdot U_1 = \frac{1}{1 - D} \cdot U_1$$

$$0 < D < 1$$

$U_1 < U_2 < \infty \leftarrow$ Only in theory. Components limit the output voltage

Step-up converter

$$I_2 \cdot t_{\text{ON}} = (I_1 - I_2) \cdot t_{\text{OFF}} \quad \Rightarrow \quad I_1 \cdot t_{\text{OFF}} = I_2 \cdot (t_{\text{ON}} + t_{\text{OFF}})$$

$$\Rightarrow \quad I_2 = I_1 \cdot \frac{T_P - t_{\text{ON}}}{T_P} = (1 - D) \cdot I_1$$

ON state ($u_{\text{CE}}(t) = U_1$):

$$-U_1 + u_L(t) = 0 \quad \Rightarrow \quad u_L(t) = U_1$$

OFF state ($u_{\text{CE}}(t) = U_2$):



$$-U_1 + u_L(t) + U_2 = 0 \quad \Rightarrow \quad u_L(t) = -(U_2 - U_1)$$

$$\overline{u_L(t)} = 0 = \frac{U_1 \cdot t_{\text{ON}} - (U_2 - U_1) \cdot t_{\text{OFF}}}{T_P} \quad \Rightarrow \quad (U_2 - U_1) \cdot t_{\text{OFF}} = U_1 \cdot t_{\text{ON}}$$


$$\Rightarrow \quad U_2 = U_1 \cdot \frac{t_{\text{OFF}} + t_{\text{ON}}}{t_{\text{OFF}}} = \frac{T_P}{t_{\text{OFF}}} \cdot U_1 = \frac{1}{1 - D} \cdot U_1$$

$$\text{next step with } L < \infty : \quad u_L(t) = L \cdot \frac{di_L}{dt}$$


Step-up converter with $L < \infty$

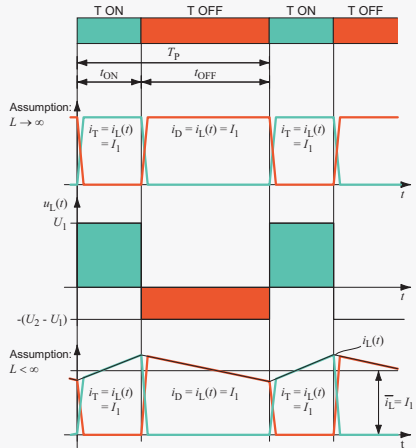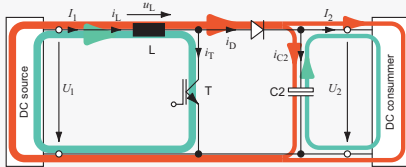


Step-up converter with $L < \infty$

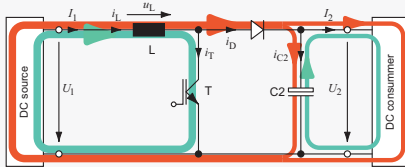

■ State ON:

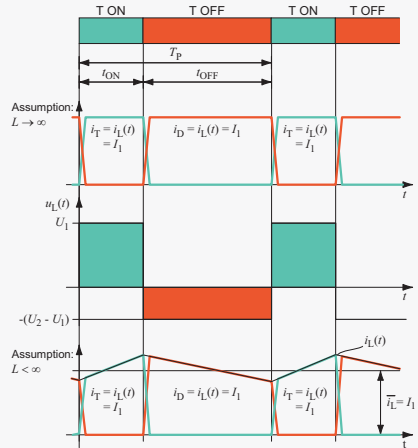


Step-up converter with $L < \infty$

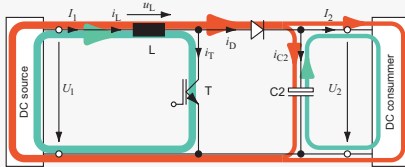


■ State ON:
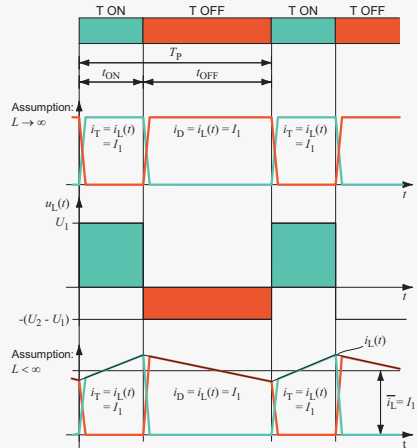
$$\blacksquare u_L(t) = U_1 = L \cdot \frac{di_L}{dt}$$




Step-up converter with $L < \infty$

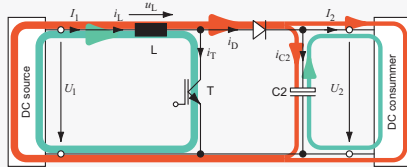


State ON:

$$u_L(t) = U_1 = L \cdot \frac{di_L}{dt}$$
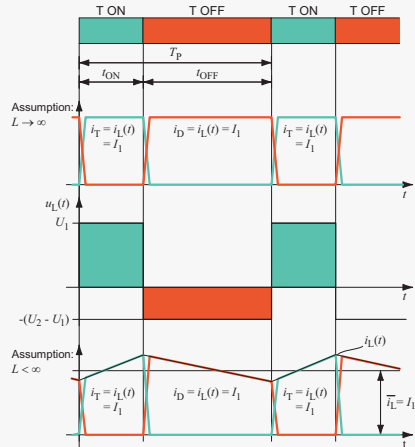
$$\Rightarrow \frac{di_L}{dt} > 0 \text{ and constant}$$



Step-up converter with $L < \infty$

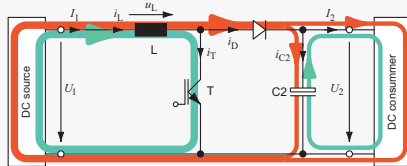


■ State ON:


$$u_L(t) = U_1 = L \cdot \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} > 0 \text{ and constant}$$

■ OFF state:

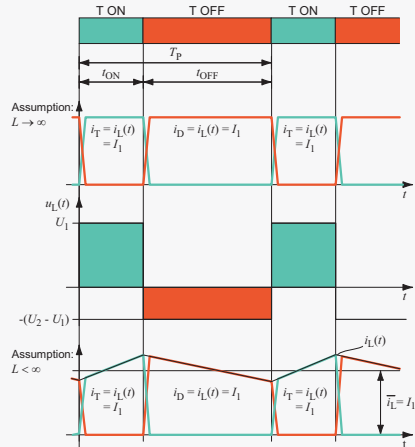

Step-up converter with $L < \infty$

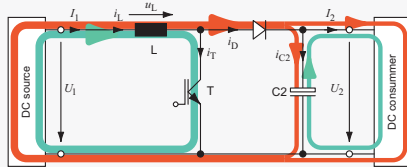


State ON:

$$u_L(t) = U_1 = L \cdot \frac{di_L}{dt}$$


$$\Rightarrow \frac{di_L}{dt} > 0 \text{ and constant}$$

OFF state:
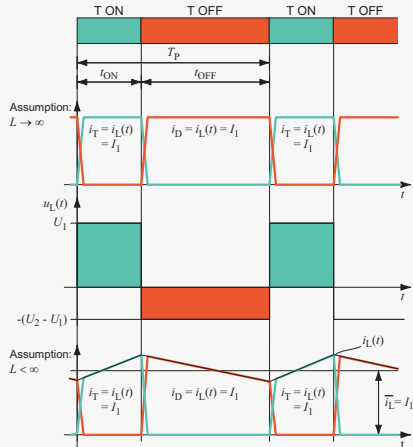
$$u_L(t) = -(U_2 - U_1) = L \cdot \frac{di_L}{dt}$$



Step-up converter with $L < \infty$

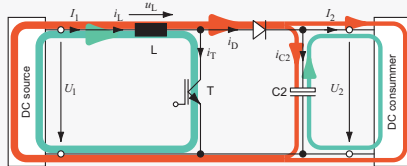

State ON:


$$u_L(t) = U_1 = L \cdot \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} > 0 \text{ and constant}$$

OFF state:

$$u_L(t) = -(U_2 - U_1) = L \cdot \frac{di_L}{dt}$$
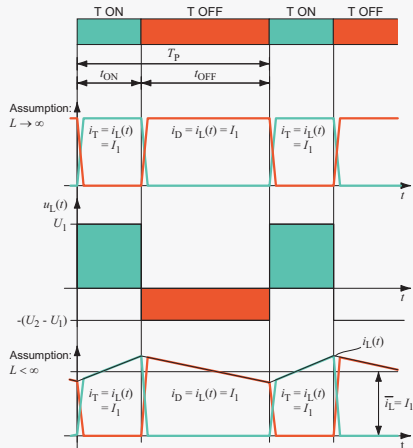
$$\Rightarrow \frac{di_L}{dt} < 0 \text{ and constant}$$



Fundamentals of power electronics for electric drives

- 1 Passive components as energy storage
- 2 Active components of power electronics
- 3 Idealization
- 4 Step-down converter (Buck-Converter)
- 5 Step-up converter (Boost-Converter)
- 6 Multi-quadrant controller**
- 7 Modulation and Inverter

Multi-quadrant controller

Step-down and step-up converters:

- Current direction at the output cannot be changed
- Voltage direction at the output cannot be changed
 - ⇒ Power can only be transferred from input to output

Multi-quadrant controller

Step-down and step-up converters:

- Current direction at the output cannot be changed
- Voltage direction at the output cannot be changed
⇒ Power can only be transferred from input to output

DC motor:

- Voltage = measure of speed
 - Current = measure of torque
- ⇒ with step-down or step-up converter only clockwise rotating motor operation
⇒ step-down or step-up converter = One-quadrant controller (1QC)



Multi-quadrant controller

Step-down and step-up converters:

- Current direction at the output cannot be changed
- Voltage direction at the output cannot be changed
 - ⇒ Power can only be transferred from input to output

DC motor:

- Voltage = measure of speed
- Current = measure of torque
- ⇒ with step-down or step-up converter only clockwise rotating motor operation
 - ⇒ step-down or step-up converter = One-quadrant controller (1QC)
- if both directions of rotation and torque are needed:
 - ⇒ both voltage AND both current directions necessary!

Multi-quadrant controller


Step-down and step-up converters:

- Current direction at the output cannot be changed
- Voltage direction at the output cannot be changed
 - ⇒ Power can only be transferred from input to output


DC motor:

- Voltage = measure of speed
- Current = measure of torque
- ⇒ with step-down or step-up converter only clockwise rotating motor operation
 - ⇒ step-down or step-up converter = One-quadrant controller (1QC)
- if both directions of rotation and torque are needed:
 - ⇒ both voltage AND both current directions necessary!
 - ⇒ Four-quadrant controller (4QC)

2 x two-quadrant controllers...

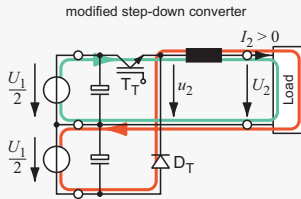


2 x two-quadrant controllers...

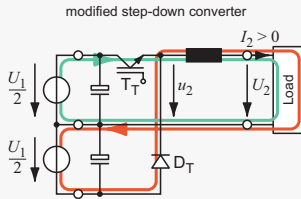


$$I_2 > 0$$

2 x two-quadrant controllers...

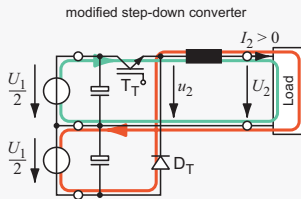



$$I_2 > 0 : \quad U_2 = -\frac{U_1}{2} \dots + \frac{U_1}{2} \quad (D = 0 \dots 1)$$

2 x two-quadrant controllers...

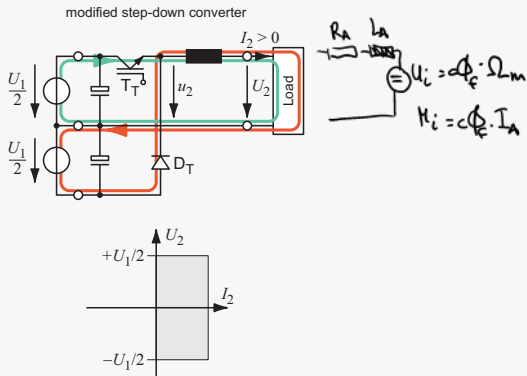

$$I_2 > 0 : \quad U_2 = -\frac{U_1}{2} \dots + \frac{U_1}{2} \quad (D = 0 \dots 1)$$



2 x two-quadrant controllers...

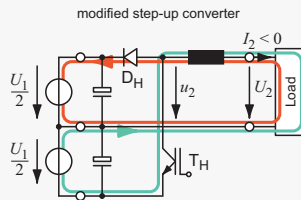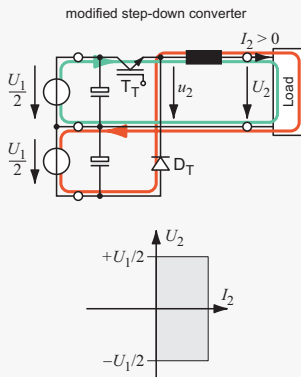


$$I_2 > 0 : \quad U_2 = -\frac{U_1}{2} \dots + \frac{U_1}{2} \quad (D = 0 \dots 1) \quad I_2 < 0$$

2 x two-quadrant controllers...

modified step-down converter

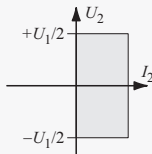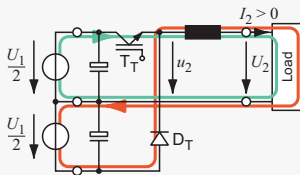


modified step-up converter

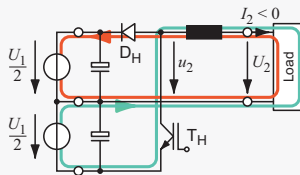

$$I_2 > 0: \quad U_2 = -\frac{U_1}{2} \dots + \frac{U_1}{2} \quad (D = 0 \dots 1) \quad I_2 < 0: \quad U_2 = +\frac{U_1}{2} \dots - \frac{U_1}{2} \quad (D = 0 \dots 1)$$

2 x two-quadrant controllers...

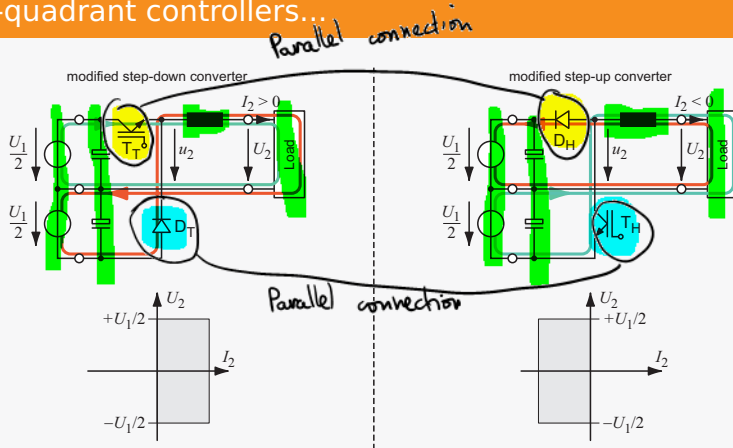

$$I_2 > 0: \quad U_2 = -\frac{U_1}{2} \dots + \frac{U_1}{2} \quad (D = 0 \dots 1) \quad I_2 < 0: \quad U_2 = +\frac{U_1}{2} \dots - \frac{U_1}{2} \quad (D = 0 \dots 1)$$

... = 1 x four-quadrant controller (half bridge)

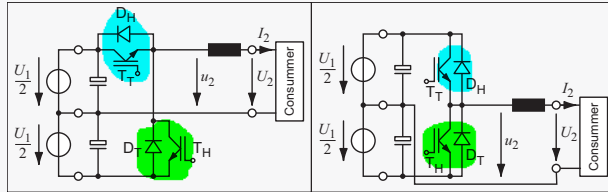


Figure Four-quadrant controller (half bridge)

- Transistors are fired alternately
- Current „finds“ its way

... = 1 x four-quadrant controller (half bridge)

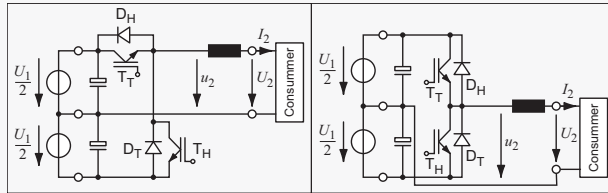


Figure Four-quadrant controller (half bridge)

- Transistors are fired alternately
- T_T fired: $U_2 > 0$
- Current „finds“ its way
- T_H fired: $U_2 < 0$

... = 1 x four-quadrant controller (half bridge)

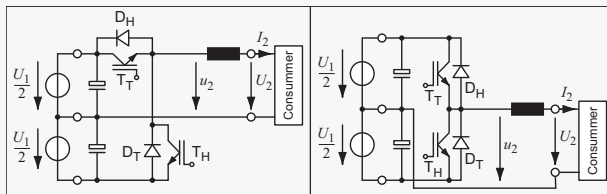


Figure Four-quadrant controller (half bridge)

- Transistors are fired alternately
- Current „finds“ its way
 - T_T fired: $U_2 > 0$
 - $I_2 > 0$: Current via T_T
 - T_H fired: $U_2 < 0$
 - $I_2 < 0$: Current via T_H
- „Drive“ ($u_L > (<)0$, $i_L > (<)0$):
 ⇒ Transistor conducts

... = 1 x four-quadrant controller (half bridge)

Already 4QC
 but with 2
 problems:

- We need
 two voltage
 sources

- Voltage source
 must be able to absorb current


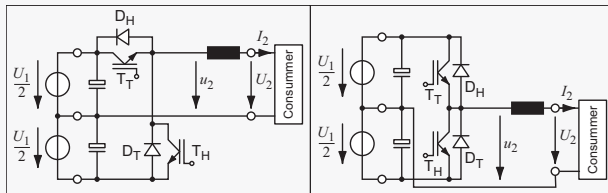



Figure Four-quadrant controller (half bridge)

- Transistors are fired alternately
- Current „finds“ its way
- „Drive“ ($u_L > (<)0$, $i_L > (<)0$):
 \Rightarrow Transistor conducts
- „Fly-back“ ($u_L > (<)0$, $i_L < (>)0$):
 \Rightarrow Diode conducts
- T_T fired: $U_2 > 0$
 - $I_2 > 0$: Current via T_T
 - $I_2 < 0$: Current via D_H
- T_H fired: $U_2 < 0$
 - $I_2 < 0$: Current via T_H
 - $I_2 > 0$: Current via D_T

2 x half-bridge = 1 x H-bridge

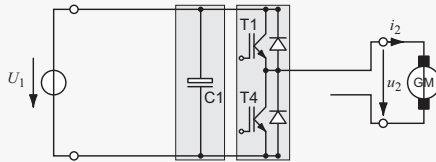


2 x half-bridge = 1 x H-bridge

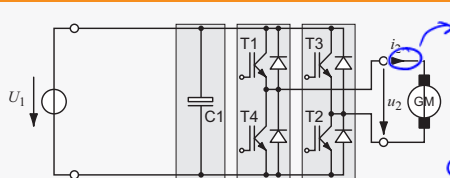

Why not a smoothing coil?
Armature inductance is often enough.
(Value of L influences $\Delta i \rightarrow$ current ripple)


- Transistors are fired in pairs (T1/T2) vs. (T3/T4).
- $i_2 > 0$: T1/T2 (drive) or D3/D4 (fly-back)

2 x half-bridge = 1 x H-bridge

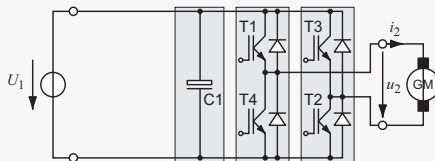

- Transistors are fired in pairs (T1/T2) vs. (T3/T4).
- $i_2 > 0$: T1/T2 (drive) or D3/D4 (fly-back)
- $i_2 < 0$: T3/T4 (drive) or D1/D2 (fly-back)

2 x half-bridge = 1 x H-bridge

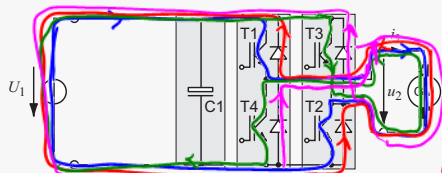


- Transistors are fired in pairs (T1/T2) vs. (T3/T4).
- $i_2 > 0$: T1/T2 (drive) or D3/D4 (fly-back)
- $i_2 < 0$: T3/T4 (drive) or D1/D2 (fly-back)

$$\overline{u_2(t)} = \frac{t_{ON}}{T_P} \cdot U_1 - \frac{t_{OFF}}{T_P} \cdot U_1$$

| | |
|------------------------------------------------------------------------------------|------------------------------------------------------------------------------------|
| ② T ₁ & T ₂ ON D ₁ & D ₂ conduct | ① T ₁ & T ₂ ON T ₁ & T ₂ conduct |
| ③ T ₃ & T ₄ ON T ₃ & T ₄ conduct | ④ T ₃ & T ₄ ON D ₃ & D ₄ ON |

$$(t_{ON} = t_{ON1} = t_{ON2} = t_{OFF3} = t_{OFF4} \quad \text{or} \quad t_{OFF} = t_{OFF1} = t_{OFF2} = t_{ON3} = t_{ON4})$$

2 x half-bridge = 1 x H-bridge

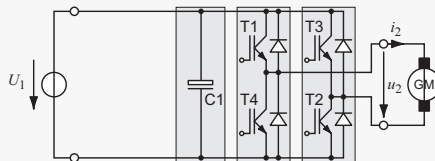


- Transistors are fired in pairs (T1/T2) vs. (T3/T4).
- $i_2 > 0$: T1/T2 (drive) or D3/D4 (fly-back)
- $i_2 < 0$: T3/T4 (drive) or D1/D2 (fly-back)

$$\overline{u_2(t)} = \frac{t_{ON}}{T_P} \cdot U_1 - \frac{t_{OFF}}{T_P} \cdot U_1 = \frac{t_{ON}}{T_P} \cdot U_1 - \frac{T_P - t_{ON}}{T_P} \cdot U_1 = \frac{2t_{ON} - T_P}{T_P} \cdot U_1$$

$$(t_{ON} = t_{ON1} = t_{ON2} = t_{OFF3} = t_{OFF4} \quad \text{or} \quad t_{OFF} = t_{OFF1} = t_{OFF2} = t_{ON3} = t_{ON4})$$

2 x half-bridge = 1 x H-bridge

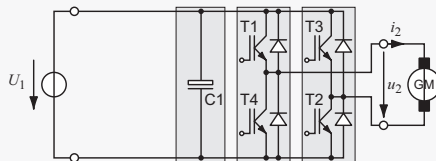


- Transistors are fired in pairs (T1/T2) vs. (T3/T4).
- $i_2 > 0$: T1/T2 (drive) or D3/D4 (fly-back)
- $i_2 < 0$: T3/T4 (drive) or D1/D2 (fly-back)

$$\overline{u_2(t)} = \frac{t_{ON}}{T_P} \cdot U_1 - \frac{t_{OFF}}{T_P} \cdot U_1 = \frac{t_{ON}}{T_P} \cdot U_1 - \frac{T_P - t_{ON}}{T_P} \cdot U_1 = \frac{2t_{ON} - T_P}{T_P} \cdot U_1 = (2D - 1) \cdot U_1$$

$$D = 0 \dots 1 : U_2 = -U_1 \dots +U_1$$

$$(t_{ON} = t_{ON1} = t_{ON2} = t_{OFF3} = t_{OFF4} \quad \text{or} \quad t_{OFF} = t_{OFF1} = t_{OFF2} = t_{ON3} = t_{ON4})$$

2 x half-bridge = 1 x H-bridge

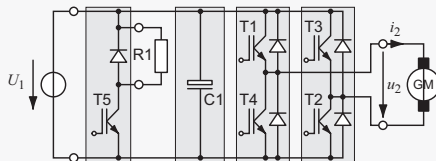

- Transistors are fired in pairs (T1/T2) vs. (T3/T4).
- $i_2 > 0$: T1/T2 (drive) or D3/D4 (fly-back)
- $i_2 < 0$: T3/T4 (drive) or D1/D2 (fly-back)
- Voltage source must be regenerative or a brake chopper is needed

$$\overline{u_2(t)} = \frac{t_{ON}}{T_P} \cdot U_1 - \frac{t_{OFF}}{T_P} \cdot U_1 = \frac{t_{ON}}{T_P} \cdot U_1 - \frac{T_P - t_{ON}}{T_P} \cdot U_1 = \frac{2t_{ON} - T_P}{T_P} \cdot U_1 = (2D - 1) \cdot U_1$$

$$D = 0 \dots 1 : U_2 = -U_1 \dots +U_1$$

$$(t_{ON} = t_{ON1} = t_{ON2} = t_{OFF3} = t_{OFF4} \quad \text{or} \quad t_{OFF} = t_{OFF1} = t_{OFF2} = t_{ON3} = t_{ON4})$$

Fundamentals of power electronics for electric drives

- 1 Passive components as energy storage
- 2 Active components of power electronics
- 3 Idealization
- 4 Step-down converter (Buck-Converter)
- 5 Step-up converter (Boost-Converter)
- 6 Multi-quadrant controller
- 7 Modulation and Inverter**


Modulation as basis for inverting

So far only „regulator “ (DC voltage in input and output) considered.


Same circuit (H-bridge) for inverting?

Pulse width modulation (PWM) \Rightarrow any form of output voltage

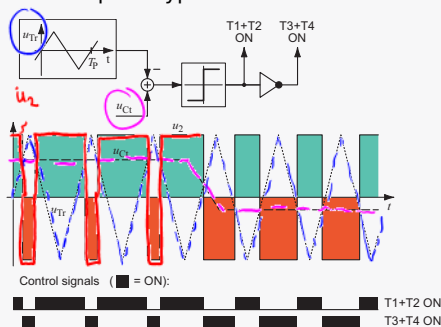
Triangle modulation: the simplest type of modulation



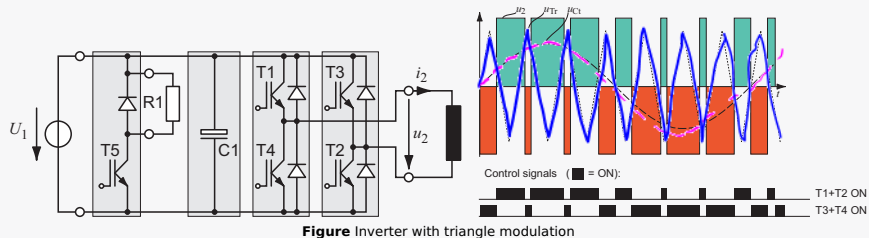Modulation of single-phase inverters (H-bridge)




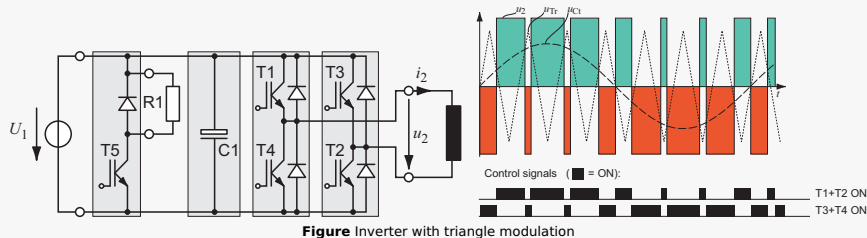Modulation of single-phase inverters (H-bridge)




- u_2 with fundamental component proportional to control voltage u_{Ct} .

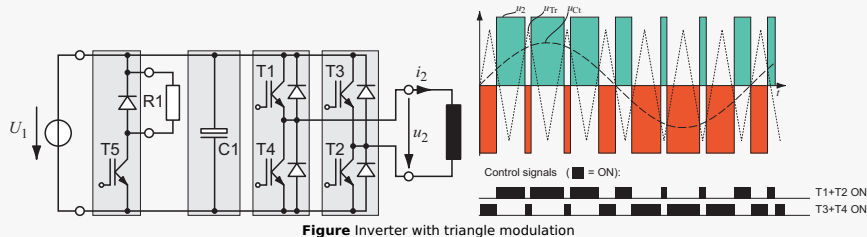Modulation of single-phase inverters (H-bridge)



- u_2 with fundamental component proportional to control voltage u_{Ct} .
- How to reduce harmonics in u_2 ? \Rightarrow Increase (pulse) switching frequency

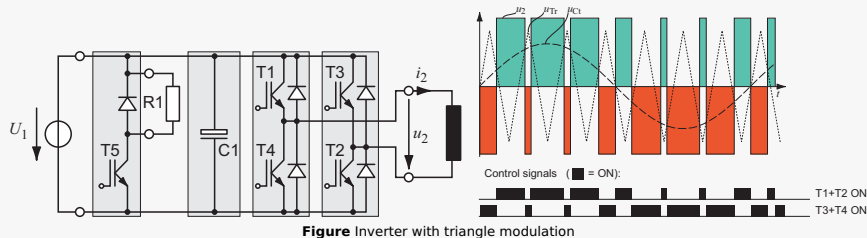Modulation of single-phase inverters (H-bridge)



- u_2 with fundamental component proportional to control voltage u_{Ct} .
- How to reduce harmonics in u_2 ? \Rightarrow Increase (pulse) switching frequency
- Limited by switching losses in the transistors

Three-phase inverter

Supply of three-phase drives: three-phase inverter

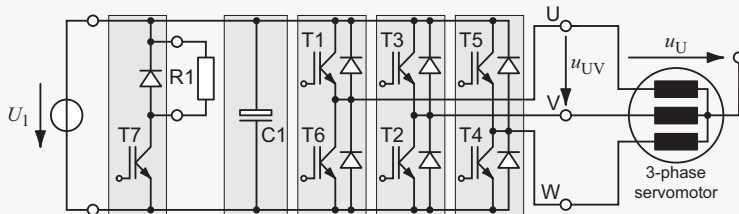


Figure Three-phase inverter with three-phase machine as load

Three-phase inverter

Supply of three-phase drives: three-phase inverter

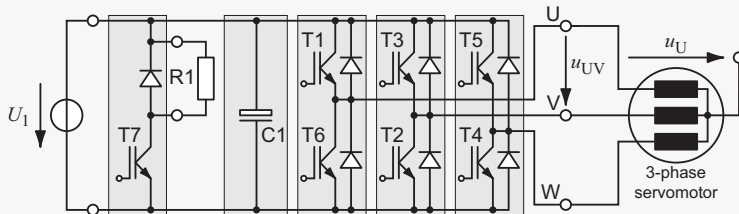


Figure Three-phase inverter with three-phase machine as load

- 120° offset on the voltages and currents

Three-phase inverter

Supply of three-phase drives: three-phase inverter

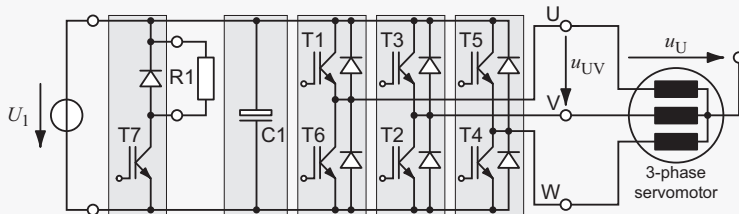


Figure Three-phase inverter with three-phase machine as load

- 120° offset on the voltages and currents
- Sum of phase currents always zero \Rightarrow only half bridges required

Three-phase inverter

Supply of three-phase drives: three-phase inverter

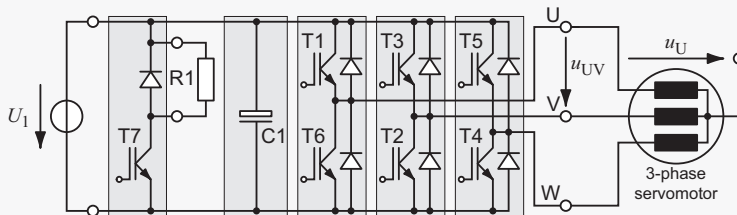


Figure Three-phase inverter with three-phase machine as load

- 120° offset on the voltages and currents
- Sum of phase currents always zero \Rightarrow only half bridges required
- Switching frequency mostly 4 kHz to 16 kHz

Three-phase inverter

Supply of three-phase drives: three-phase inverter

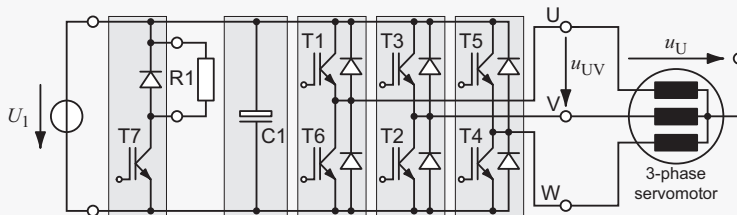


Figure Three-phase inverter with three-phase machine as load

- 120° offset on the voltages and currents
- Sum of phase currents always zero \Rightarrow only half bridges required
- Switching frequency mostly 4 kHz to 16 kHz
- Space vector modulation (voltage in d and q axis) instead of triangular modulation (phase voltages) \Rightarrow higher output voltage

Given the circuit and values in Figure 7.22. The idealized theory is assumed with the exception of a finitely large inductor.

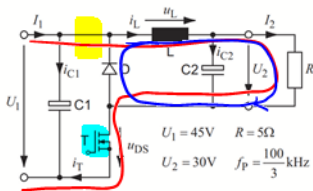


Figure 7.22: DC converter

u_2, I_2, u_1, I_1 are constants
 i_L is not a constant
 $\bar{u}_L = 0, \bar{i}_c = 0$

T ON: $U_1 = U_L + U_2$
 $\Rightarrow U_L = U_1 - U_2 = 15V$

T OFF: $0 = u_1 + u_2$

$$u_L = -u_2 = -30V$$

- Which basic converter type corresponds to this circuit?
How was it varied?
- Determine the DC input current I_1 , the DC output current I_2 , the on-time t_{ON} and the off-time t_{OFF} for the MOSFET T. How big is the inductor L if its current i_L may only vary by $\pm 0.5 \text{ A}$?

a) Buck or Step-down converter

$$- u_2 < u_1$$

- T is in series and D in parallel

Difference? T is in series with the negative terminal instead of with the positive

b) I_1 ? I_2 ? t_{on} ? t_{off} ?

$$I_2 = \frac{U_2}{R_2} = \frac{30V}{5\Omega} = 6A$$

No losses in the circuit $\Rightarrow U_1 \cdot I_1 = U_2 \cdot I_2$

$$I_1 = \frac{U_2 I_2}{U_1} = \frac{30V \cdot 6A}{45V} = 4A$$

$$D = \frac{U_2}{U_1} = \frac{I_1}{I_2} = \frac{30V}{45V} = \frac{2}{3} = \frac{t_{on}}{T_p} = t_{on} \cdot f_p$$

Equation only
valid for step-down
converter

$$t_{on} = \frac{2}{3} \cdot \frac{1}{f_p} = \frac{2}{3} \cdot \frac{1}{100/3 \text{ kHz}} = 20\mu s$$



$$(T_p = \frac{1}{f_p} = \frac{1}{100/3 \text{ kHz}} = 30\mu s) \quad t_{off} = T_p - t_{on} = T_p(1-D) = 10\mu s$$

$$\begin{aligned} \text{T ON: } u_1 &= u_L + u_2 \\ \Rightarrow u_L &= u_1 - u_2 = 15\text{V} \end{aligned}$$

$$\begin{aligned} \text{T OFF: } 0 &= u_L + u_2 \\ u_L &= -u_2 = -30\text{V} \end{aligned}$$

$$u_L = L \cdot \frac{di_L}{dt}$$
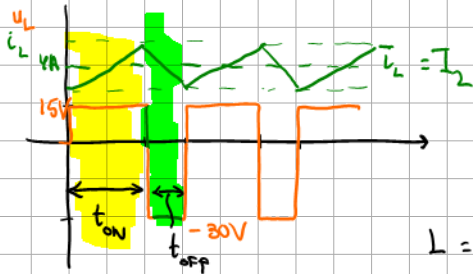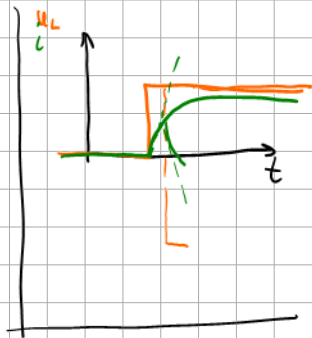
$$u_L = L \cdot \frac{\Delta i_L}{\Delta t}$$



$$\Rightarrow \Delta i_L = \pm 0.5 \text{ A} = 1 \text{ A}$$

$$\begin{aligned} L &= \frac{u_L \cdot \Delta t}{\Delta i_L} = \frac{15\text{V} \cdot 20 \cdot 10^{-6} \text{s}}{1 \text{A}} = \frac{-30\text{V} \cdot 10 \cdot 10^{-6} \text{s}}{-1 \text{A}} \\ L &= 0.3 \text{ mH} \end{aligned}$$

Example 7-5: H-bridge

Given is the four-quadrant controller shown in Figure 7.26 with an oscillographed current curve.

- Fill in the table!
- What is the counter induced voltage U_G and the inductor L ?

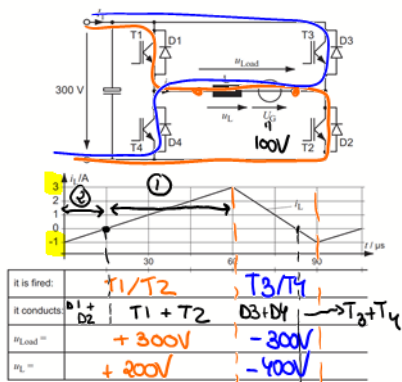


Figure 7.26: four-quadrant controller

$$u_L = L \frac{di_L}{dt} = L \frac{\Delta i_L}{\Delta t}$$

if: $\frac{\Delta i_L}{\Delta t} > 0 \rightarrow u_L > 0$


T1 & T2 ON

if $i_L > 0$ T1 & T2 conduct
 $i_L < 0$ D3 & D4 conduct

$$\frac{\Delta i_L}{\Delta t} < 0 \rightarrow u_L < 0$$

T3 & T4 ON

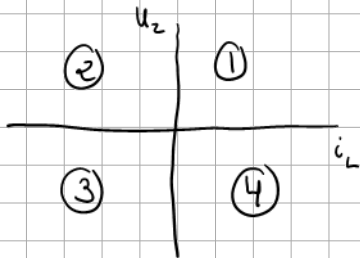if $i_L < 0$ T3 & T4 conduct
 $i_L > 0$ D3 & D4 conduct



$$u_L = u_{\text{Load}} - u_G \rightarrow u_G?$$

$$\cancel{\bar{u}_L} = \bar{u}_{\text{Load}} - u_G \rightarrow u_G = \bar{u}_{\text{Load}} = \frac{1}{90\mu\text{s}} \cdot (300\text{V} \cdot 60\mu\text{s} - 300\text{V} \cdot 30\mu\text{s})$$

$$= 100\text{V}$$

$$u_L = L \cdot \frac{\Delta i_L}{\Delta t} \rightarrow L = \frac{200\text{V} \cdot 60\mu\text{s}}{4\text{A}} = \underline{\underline{3\text{mH}}}$$

